



University of Bahrain

College of Information Technology

Department of Computer Engineering

ITCE364 – Section 01

Final Project

VHDL Design of a 1-Bus Processor with a Hardwired Control Unit

Monitored by: Dr. Jalal Khlaifat

Prepared by:

Weaam Wafeeq Ajoor - ID: 20196537

Puja Karmakar - ID: 20194981

Zainab Redha Matrook - ID: 20195982

Due Date: 24 May 2022

Table of Contents

Objectives.....	4
Research Plan	4
Table of Tasks	4
Tasks Distribution among Members	4
Timeline	5
Introduction.....	6
Processor Description	7
Processor Specifications & Design logic Description	7
Components Block Diagram	8
ALU Component.....	8
Memory Component.....	8
Register File Component.....	9
Control Unit Component.....	9
Datapath Component	10
Instructions' Format.....	11
Concrete RTN:	14
Implementation	18
ALU Unit Component.....	18
Register File Component	19
Memory Unit Component	20
Control Unit Component.....	21
.....	22
Data Path Component	23
.....	24
Results	25
Components RTL	25
ALU Unit Component	25
Memory Unit Component.....	26
Register File Component.....	27

.....	27
Control Unit Component.....	29
.....	29
Data Path Component.....	31
.....	31
Components Simulation	32
ALU Unit Component	32
Register File Component.....	34
Memory Unit Component.....	36
Control Unit Component.....	37
Conclusion	40

Objectives

- VHDL code to implement 1-bus processor with a hardwired control unit that have specific characteristic.
- Simulate each component and test their functionality.
- Write a top level code to connect all components as a one system.

Research Plan

Table of Tasks

	Table of Tasks
1	Discuss each component functionality
2	Examine how all the components are connected to each other
3	Identify the RTN for all the instructions
4	Research and Code for ALU
5	Research and Code for Register File
6	Research and Code for Memory
7	Research and Code for Control Unit
8	Research and Code for Data Path
9	Ask the mentor for any further help
10	Debugging Errors for all the components
11	Simulate and test the components functionality
12	Writing the Research Report
13	Preparing the Presentation slides

Tasks Distribution among Members

All the tasks were executed by all of the team members since multiple online meetings on Teams software were arranged to ensure that there is team collaboration.

Timeline



Week 10-16 April 2022

Arrange couple of meetings to discuss components needed for the processor. By the end of the week, the group are need to make sure to know how these components are connected to each other.

Week 12-23 April 2022

Search and gather the RTN required for all the instructions mentioned in the processor specification. Then, the team members will start coding for the control unit, and ALU. The codes will be compiled, errors will be debugged and simulate the components.

Week 24-30 April 2022

The team members will then start coding for the register file and memory. Each code will be compiled, errors will be debugged, and simulate the components.

Week 8-14 May 2022

Throughout this week the team members will focus on the data path component. Throughout this component all the other component will be connected and port mapped. After writing the code, it will be compiled, errors will be debugged, and component will be simulated.

Week 15-23 May 2022

Work on the Research Report.

In addition, the team member will prepare the presentation slides.

Introduction

A common analogy used for describing a computer's processor (CPU) is thinking of the computer like a human body and the CPU is its brain. The term "Processor" refers to the CPU. The CPU is in charge of processing the computer's tasks by constantly resolving mathematical and logical problems. A computer would have at least one CPU which is usually divided into a Control Unit, Data path, buses, and temporary storage. The control unit (CU) is responsible to organize and fetch the CPU instructions and generating "Control Signals" that control the data path and tell the ALU, memory, and input/output devices what to do. Control units can be divided into two types: "Microprogrammed based control unit" and "Hardwired based controlled Unit". Microprogrammed-based control unit treats the relationship between control inputs and outputs as a memory system. Where the memory contains control signals that are stored as "words". During instruction execution at each clock tick, the required "word" is fetched from memory to supply the control signals. Whereas, Hardwired-based controlled Unit treats the relationship between control inputs and outputs as a series of Boolean functions, one for each control signal. Moving to the Data path, it contains CPU registers and ALU. ALU is in charge of performing arithmetic operations and logical functions. While the "bus" is an interconnection through which voltage signals will be flowing and the bus can be used for a different purpose. If the bus carries an address it is known as "Address Bus", if it is carrying any data it is known as "Data Bus", and if it is carrying control signals it is known as "Control signals". There are three types of bus organization for the data bus One-Bus Organization (only one operand can be fetched from this bus), Two-Bus Organization (two operands can be fetched from this bus, one is used for fetching the register, and one for the ALU), and Three-Bus Organization (three operands can be fetched from this bus). Finally, a temporary storage unit such as register files or latches is used to provide easy access to data within the CPU.


Thus, this project will focus on the implementation of a 1-bus processor with a hardwired control unit and specific characteristics. The report was categorized into three chapters as follows. Chapter 1 illustrates the Processor specifications, design logic description, instructions' format & RTN, and control signals declaration. Chapter 2 emphasizes the code that has been accomplished. Chapter 3 draws the focus on simulation and results.

Processor Description

Processor Specifications & Design logic Description


- 1-bus processor with hardwired control unit
- 32 -bit Data Bus
- 32 -bit Address Bus
- 32 -bit Program Counter (PC).
- 32 -bit Instruction Register (IR).
- 24 general purpose registers.
- SRC has 13 different instructions each with different format. The Instructions are: **Add, Or, Sub, And, Addi , Ld, St, Lar, Brpl, Brmi, Stop, Nop, Shc.** (The Shift Circular instruction execute within one clock cycle)

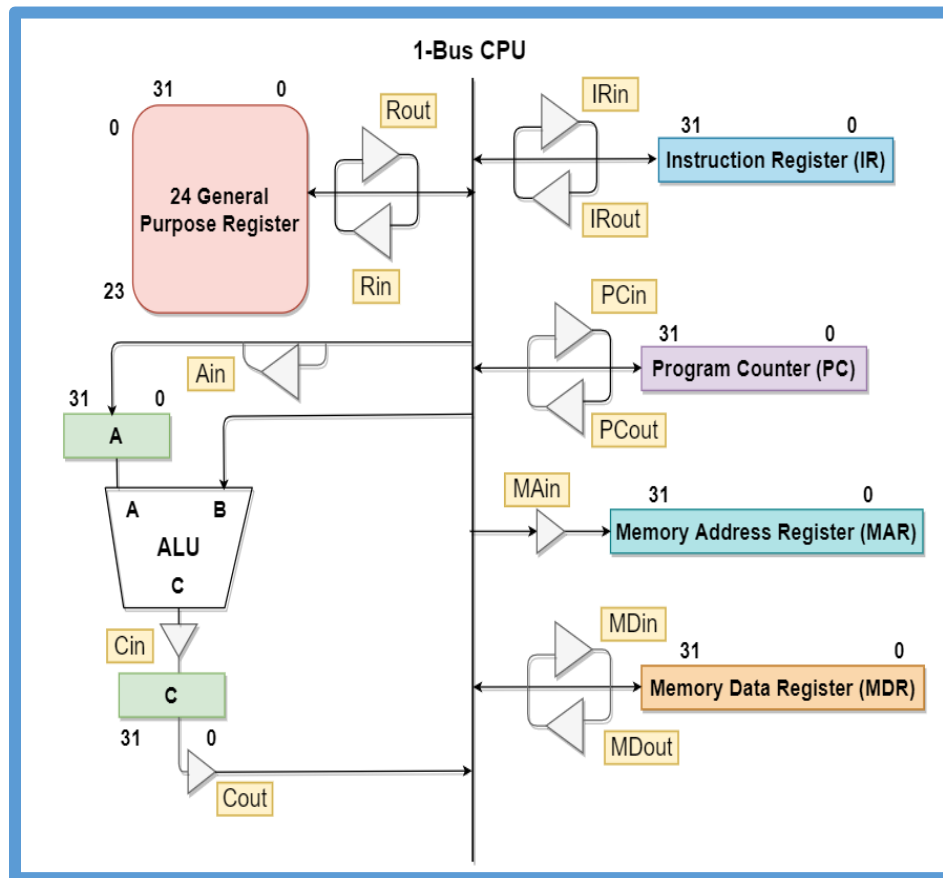The following block diagram illustrates the top level view of the processor:




Components Block Diagram


ALU Component

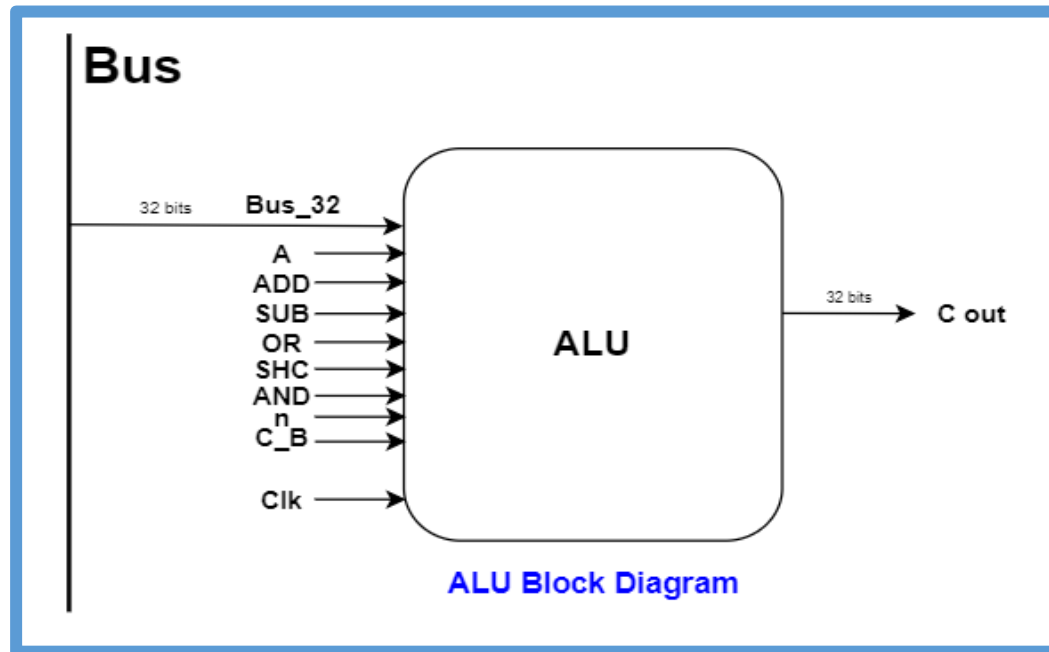


Memory Component

 


Register File Component

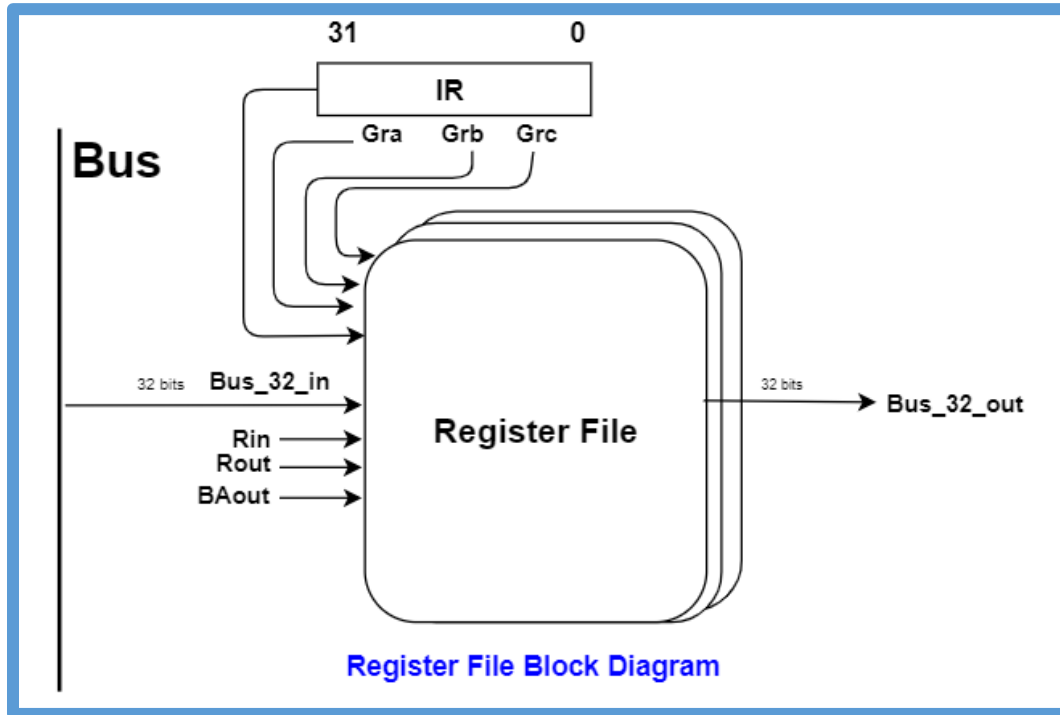

Control Unit Component

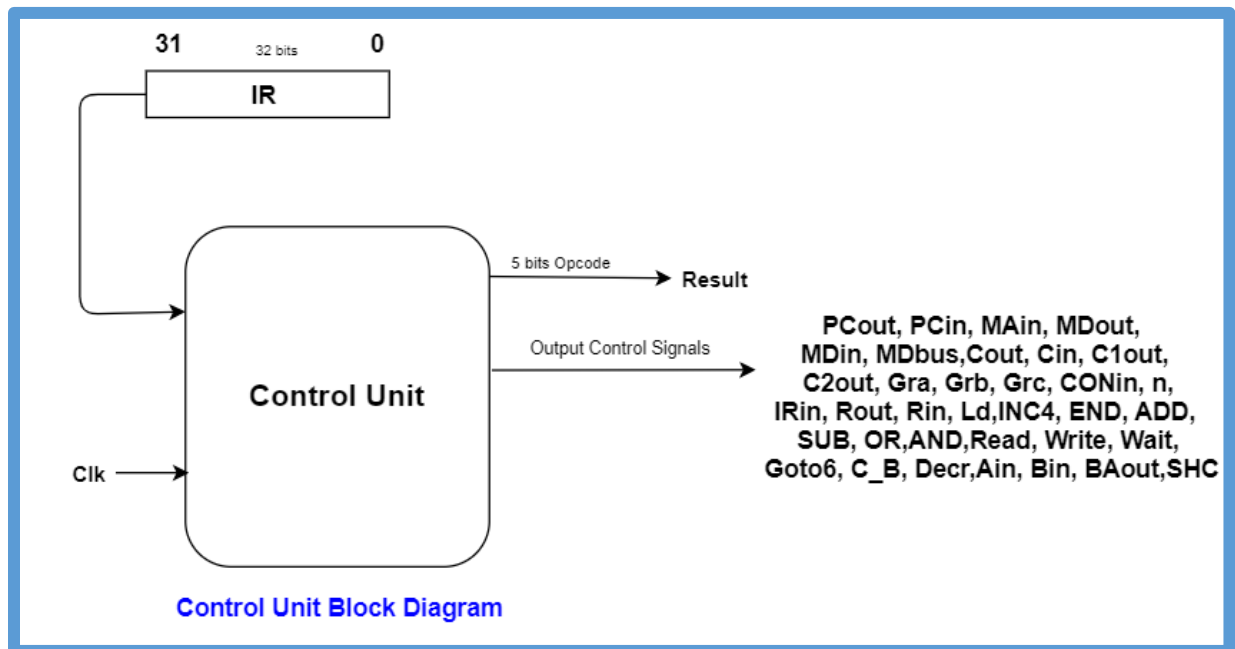

Datapath Component

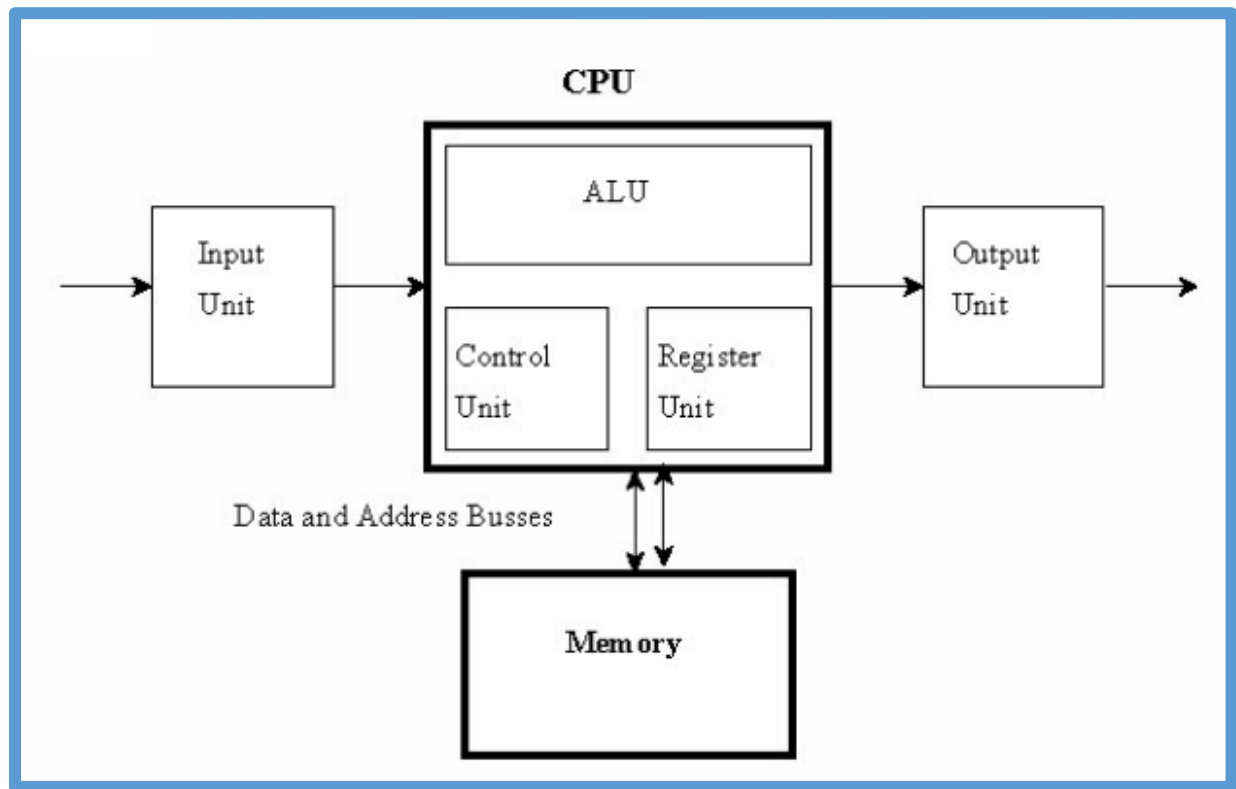

Instructions' Format

All instructions are 32-bits long, 5-bits are used for opcode field and 27-bits for IR instructions.


The following table defines the 13 instructions:

Opcode	Value	Instructions Declaration
Nop	0	Used as placeholder or time waster
Ld	1	Loads value to a specific location in register addressed.
st	3	Store the value of the register to the given memory address
lar	6	Add the PC value to the constant value that will to uploaded to a specific location in register addressed
add	12	Add the value in the register with the given value.
addi	13	Performs an addition on both the source register's contents and the immediate data, and stores the result in the destination register.
sub	14	Subtract the value of the register from the given value
brlpl	18	It checker whether the most significant bit of the value in the register is positive or not. If it is positive then the PC value will be copied to “linkage register” and jump to targeted address.
brlmi	19	It checker whether the most significant bit of the value in the register is negative or not. If it is negative then the PC value will be copied to “linkage register” and jump to targeted address.


and	20	And-ing the value of the register from the given value.
or	22	Or-ing the value of the register from the given value.
shc	29	Shift the bits of the value found in the register 'n' time circular way, from the left till the right and vice versa.
Stop	31	Halt the machine

These instructions will have the following format:


1. Nop, Stop

 


2. Addi, Ld, St

 


3. Lar

 


4. Add, Or, Sub, And,

 

5. Shc

 

6. Brlpl, Brlmi

 

Concrete RTN:

1- NOP Instruction (Opcode =0):

Time	Concrete RTN	Control Signals
T0	$MA \leftarrow PC: C \leftarrow PC+4$	$PC_{out}, MA_{in}, INC4, C_{in}$
T1	$MD \leftarrow M[MA]: PC \leftarrow C$	Read, Wait, $C_{out}, PC_{in},$
T2	$IR \leftarrow MD$	MD_{out}, IR_{in}

2- Ld Instruction (Opcode =1):

Time	Concrete RTN	Control Signals
T0	$MA \leftarrow PC: C \leftarrow PC+4$	$PC_{out}, MA_{in}, INC4, C_{in}$
T1	$MD \leftarrow M[MA]: PC \leftarrow C$	Read, Wait, $C_{out}, PC_{in},$
T2	$IR \leftarrow MD$	MD_{out}, IR_{in}
T3	$(rb \neq 0) \rightarrow (A \leftarrow 0)$ $(rb \neq 0) \leftarrow (A \leftarrow R[rb])$	G_{rb}, BA_{out}, A_{in}
T4	$C \leftarrow A + C_2 \{sign\ Ext\}$	C_{2out}, Add, C_{in}
T5	$MA \leftarrow C$	C_{out}, MA_{in}
T6	$MD \leftarrow M[MA]$	Read, Wait
T7	$R[ra] \leftarrow MD$	$MD_{out}, G_{rb}, R_{in}, END$

3- St Instruction (Opcode =3):

Time	Concrete RTN	Control Signals
T0	$MA \leftarrow PC: C \leftarrow PC+4$	$PC_{out}, MA_{in}, INC4, C_{in}$
T1	$MD \leftarrow M[MA]: PC \leftarrow C$	Read, Wait, C_{out}, PC_{in} ,
T2	$IR \leftarrow MD$	MD_{out}, IR_{in}
T3	$(rb \neq 0) \rightarrow (A \leftarrow 0)$ $(rb \neq 0) \leftarrow (A \leftarrow R[rb])$	G_{rb}, BA_{out}, A_{in}
T4	$C \leftarrow A + C_2 \{sign\ Ext\}$	C_{2out}, Add, C_{in}
T5	$MA \leftarrow C$	C_{out}, MA_{in}
T6	$MD \leftarrow R[ra]$	$G_{ra}, R_{out}, MD_{bus}$
T7	$M[MA] \leftarrow MD$	Wait, Wait, END.

4- Lar Instruction (Opcode =6):

Time	Concrete RTN	Control Signals
T0	$MA \leftarrow PC: C \leftarrow PC+4$	$PC_{out}, MA_{in}, INC4, C_{in}$
T1	$MD \leftarrow M[MA]: PC \leftarrow C$	Read, Wait, C_{out}, PC_{in} ,
T2	$IR \leftarrow MD$	MD_{out}, IR_{in}
T3	$A \leftarrow PC$	PC_{out}, A_{in}
T4	$C \leftarrow A + C_1 \{sign\ Ext\}$	C_{1out}, ADD, C_{in}
T5	$R[ra] \leftarrow C$	$C_{out}, G_{ra}, R_{in}, END.$

5- Add Instruction (Opcode =12):

Time	Concrete RTN	Control Signals
T0	$MA \leftarrow PC: C \leftarrow PC+4$	$PC_{out}, MA_{in}, INC4, C_{in}$
T1	$MD \leftarrow M[MA]: PC \leftarrow C$	Read, Wait, C_{out}, PC_{in} ,
T2	$IR \leftarrow MD$	MD_{out}, IR_{in}
T3	$A \leftarrow R[rb]$	G_{rb}, R_{out}, A_{in}
T4	$C \leftarrow A + R[rc]$	$G_{rc}, R_{out}, ADD, C_{in}$
T5	$R[ra] \leftarrow C$	$C_{out}, G_{ra}, R_{in}, END.$

6- Addi Instruction (Opcode =13):

Time	Concrete RTN	Control Signals
T0	$MA \leftarrow PC:C \leftarrow PC+4$	$PC_{out}, MA_{in}, INC4, C_{in}$
T1	$MD \leftarrow M[MA]:PC \leftarrow C$	Read, Wait, C_{out}, PC_{in} ,
T2	$IR \leftarrow MD$	MD_{out}, IR_{in}
T3	$A \leftarrow R[rb]$	G_{rb}, R_{out}, A_{in}
T4	$C \leftarrow A + R[rc]$	C_{2out}, ADD, C_{in}
T5	$R[ra] \leftarrow C$	$C_{out}, G_{ra}, R_{in}, END.$

7- Sub Instruction (Opcode =14):

Time	Concrete RTN	Control Signals
T0	$MA \leftarrow PC:C \leftarrow PC+4$	$PC_{out}, MA_{in}, INC4, C_{in}$
T1	$MD \leftarrow M[MA]:PC \leftarrow C$	Read, Wait, C_{out}, PC_{in} ,
T2	$IR \leftarrow MD$	MD_{out}, IR_{in}
T3	$A \leftarrow R[rb]$	G_{rb}, R_{out}, A_{in}
T4	$C \leftarrow A + R[rc]$	$G_{rc}, R_{out}, SUB, C_{in}$
T5	$R[ra] \leftarrow C$	$C_{out}, G_{ra}, R_{in}, END.$

8- Brlpl & Brlpl Instruction (Opcode =18 & 19):

Time	Concrete RTN	Control Signals
T0	$MA \leftarrow PC:C \leftarrow PC+4$	$PC_{out}, MA_{in}, INC4, C_{in}$
T1	$MD \leftarrow M[MA]:PC \leftarrow C$	Read, Wait, C_{out}, PC_{in} ,
T2	$IR \leftarrow MD$	MD_{out}, IR_{in}
T3	$A \leftarrow PC$	G_{rb}, R_{out}, A_{in}
T4	$C \leftarrow A + C_1\{\text{sign Ext}\}$	C_{1out}, ADD, C_{in}
T5	$R[ra] \leftarrow C$	$C_{out}, G_{ra}, R_{in}, END.$

9- And Instruction (Opcode =20):

Time	Concrete RTN	Control Signals
T0	$MA \leftarrow PC:C \leftarrow PC+4$	$PC_{out}, MA_{in}, INC4, C_{in}$
T1	$MD \leftarrow M[MA]:PC \leftarrow C$	Read, Wait, C_{out}, PC_{in} ,
T2	$IR \leftarrow MD$	MD_{out}, IR_{in}
T3	$A \leftarrow R[rb]$	Grb, R_{out}, A_{in}
T4	$C \leftarrow A \wedge R[rc]$	$Grc, R_{out}, AND, C_{in}$
T5	$R[ra] \leftarrow C$	$C_{out}, Gra, R_{in}, END.$

10- OR Instruction (Opcode =22):

Time	Concrete RTN	Control Signals
T0	$MA \leftarrow PC:C \leftarrow PC+4$	$PC_{out}, MA_{in}, INC4, C_{in}$
T1	$MD \leftarrow M[MA]:PC \leftarrow C$	Read, Wait, C_{out}, PC_{in} ,
T2	$IR \leftarrow MD$	MD_{out}, IR_{in}
T3	$A \leftarrow R[rb]$	Grb, R_{out}, A_{in}
T4	$C \leftarrow A \vee R[rc]$	Grc, R_{out}, OR, C_{in}
T5	$R[ra] \leftarrow C$	$C_{out}, Gra, R_{in}, END.$

11- SHC Instruction (Opcode =29):

Time	Concrete RTN	Control Signals
T0	$MA \leftarrow PC:C \leftarrow PC+4$	$PC_{out}, MA_{in}, INC4, C_{in}$
T1	$MD \leftarrow M[MA]:PC \leftarrow C$	Read, Wait, C_{out}, PC_{in} ,
T2	$IR \leftarrow MD$	MD_{out}, IR_{in}
T3	$n \rightarrow IR <4..0>$	$C1_{out}, Ld$
T4	$(n=0) \rightarrow (n \leftarrow R[rc] <4..0>)$	$(n=0) \rightarrow (Grc, R_{out}, Ld)$
T5	$C \leftarrow R[rc]$	$Grb, R_{out}, C=B, C_{in}$
T6	$Shc := (n \neq 0) \rightarrow$ $(C \leftarrow C <30..0> \# C <31> :$ $n \leftarrow n-1; Shc));$	$(n \neq 0) \rightarrow (C_{out}, SHC, C_{in},$ Decr, Goto6)
T7	$R[ra] \leftarrow C$	$C_{out}, Gra, R_{in}, END.$

Implementation

This section will cover the code accomplished for each and every component.

ALU Unit Component

```
1  Library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5  use ieee.std_logic_1164.all;
6
7  entity ALU is
8      port
9      (
10         clk: in    std_logic;
11         Bus_32: in  std_logic_vector (31 downto 0);
12         A: in  std_logic_vector (31 downto 0);
13         n, ADD, SUB, AND_sig, OR_sig, SHC, C_B, INC4: in std_logic;
14         C: out std_logic_vector (31 downto 0)
15     );
16
17 end ALU;
18
19
20 architecture Behavioral of ALU is
21     signal C_sig: std_logic_vector(31 downto 0);
22     begin
23
24     process (clk, n, ADD, SUB, AND_sig, OR_sig, SHC, C_B, INC4)
25     begin
26         if (clk'event AND clk = '1') then
27             if (ADD='1') then
28                 C_sig<=Bus_32 + A;
29
30             elsif (SUB='1') then
31                 C_sig<=Bus_32 - A;
32
33             elsif (INC4='1') then
34                 C_sig<=Bus_32 + 4;
35
36             elsif (AND_sig='1') then
37                 C_sig<=A and Bus_32;
38
39             elsif (OR_sig='1') then
40                 C_sig<=A or Bus_32;
41
42             elsif (SHC='1') then
43                 if (n='0') then --no shift circular is operated when n=0
44                     C<= C_sig;
45                 else
46                     C_sig<= (C_sig(30 downto 0)& C_sig(31));
47                 end if;
48
49             elsif (C_B='1') then
50                 C_sig<= Bus_32;
51
52             end if;
53         end if;
54         C<= C_sig;
55     end process;
56 end behavioral;
```

Successful Compilation of ALU Component:

ALU.vhd		Compilation Report - control_unit	
Table of Contents		Flow Summary	
Flow Summary		<<Filter>>	
Flow Settings		Flow Status	Successful - Sun May 22 22:56:33 2022
Flow Non-Default Global Settings		Quartus Prime Version	17.1.0 Build 590 10/25/2017 SJ Lite Edition
Flow Elapsed Time		Revision Name	control_unit
Flow OS Summary		Top-level Entity Name	ALU
Flow Log		Family	MAX 10
> Analysis & Elaboration		Device	10M08DAF256C7G
Flow Messages		Timing Models	Final
Flow Suppressed Messages		Total logic elements	N/A until Partition Merge
		Total registers	N/A until Partition Merge
		Total pins	N/A until Partition Merge
		Total virtual pins	N/A until Partition Merge
		Total memory bits	N/A until Partition Merge
		Embedded Multiplier 9-bit elements	N/A until Partition Merge
		Total PLLs	N/A until Partition Merge
		UFM blocks	N/A until Partition Merge
		ADC blocks	N/A until Partition Merge

Register File Component

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.numeric_std.ALL;
4
5
6 entity register_file is
7     Port (
8         Bus_32_in : in STD_LOGIC_VECTOR (31 downto 0) := x"00000000";
9         Rin : in STD_LOGIC;
10        Rout : in STD_LOGIC;
11        BAout : in STD_LOGIC;
12        Gra : in STD_LOGIC;
13        Grb : in STD_LOGIC;
14        Grc : in STD_LOGIC;
15        IR : in STD_LOGIC_VECTOR (31 downto 0) := x"00000000";
16        Bus_32_out : out STD_LOGIC_VECTOR (31 downto 0)
17    );
18 end register_file;
19
20 architecture Behavioral of register_file is
21     signal reg : std_logic_vector (4 downto 0);
22     type reg_array is array(0 to 23) of std_logic_vector(31 downto 0);
23     signal myreg : reg_array := (x"00000000", x"00000001", x"00000002", x"00000003", x"00000004", x"00000005", x"00000006",
24     x"00000007", x"00000008", x"00000009", x"00000010", x"00000011", x"00000012", x"00000013", x"00000014", x"00000015",
25     x"00000016", x"00000017", x"00000018", x"00000019", x"00000020", x"00000021", x"00000022", x"00000023");
26
27 begin
28
29     Bus_32_out <= x"00000000" when (BAout = '1' and Grb = '1' and IR(21 downto 17) = "00000") else
30     myreg(to_integer(unsigned(IR(21 downto 17)))) when (BAout = '1' and Grb = '1' and IR(21 downto 17) /= "00000") else
31     myreg(to_integer(unsigned(IR(26 downto 22)))) when (Rout = '1' and Gra = '1') else
32     myreg(to_integer(unsigned(IR(21 downto 17)))) when (Rout = '1' and Grb = '1') else
33     myreg(to_integer(unsigned(IR(16 downto 12)))) when (Rout = '1' and Grc = '1');
34
35
36     Reg <= IR(26 downto 22) when Gra = '1' else
37     IR(21 downto 17) when Grb = '1' else
38     IR(16 downto 12) when Grc = '1' else
39     IR(26 downto 22); -- default value.
40
41     myreg(to_integer(unsigned(Reg))) <= Bus_32_in when (Rin = '1');
42
43 end Behavioral;
```

Successful Compilation of Register File Component:

Compilation Report - control_unit		register_file.vhd
Table of Contents		Flow Summary
Flow Summary		<<Filter>>
Flow Settings		Flow Status Successful - Mon May 23 01:46:15 2022
Flow Non-Default Global Settings		Quartus Prime Version 17.1.0 Build 590 10/25/2017 SJ Lite Edition
Flow Elapsed Time		Revision Name control_unit
Flow OS Summary		Top-level Entity Name register_file
Flow Log		Family MAX 10
> Analysis & Elaboration		Device 10M08DAF256C7G
Flow Messages		Timing Models Final
Flow Suppressed Messages		Total logic elements N/A until Partition Merge
		Total registers N/A until Partition Merge
		Total pins N/A until Partition Merge
		Total virtual pins N/A until Partition Merge
		Total memory bits N/A until Partition Merge
		Embedded Multiplier 9-bit elements N/A until Partition Merge
		Total PLLs N/A until Partition Merge
		UFM blocks N/A until Partition Merge
		ADC blocks N/A until Partition Merge

Memory Unit Component

```
1
2  Library ieee;
3  use ieee.std_logic_unsigned.all;
4  use ieee.std_logic_1164.all;
5  use ieee.std_logic_arith.all;
6
7
8  entity memory is
9  |
10 |   port
11 |   (clk: in std_logic;
12 |    MAin: in std_logic;
13 |    MDin, MDout, write_sig, read_sig: in std_logic;
14 |    datain: in std_logic_vector(31 downto 0); --input of MA
15 |    dataout: out std_logic_vector(31 downto 0); --output of MA
16 |    dataout1: out std_logic_vector(31 downto 0)
17 |   );
18  end memory;
19
20
21  architecture Behavioral of memory is
22  |
23  |   signal data : std_logic_vector (31 downto 0);
24  |
25  |   begin
26  |   process (write_sig, read_sig, MDout, clk, MAin, MDin)
27  |   |
28  |   |   begin
29  |   |   |   if (clk'event AND clk = '1') then
30  |   |   |   |   if (MAin='1') then
31  |   |   |   |   |   data <= datain;
32  |   |   |   |   |   elsif (MDin='1') then
33  |   |   |   |   |   |   data <= datain1;
34  |   |   |   |   |   |   elsif (MDout = '1') then
35  |   |   |   |   |   |   |   dataout1 <= data;
36  |   |   |   |   |   |   |   End if;
37  |   |   |   |   |   |   |
38  |   |   |   |   |   |   |   If (write_sig = '1') then
39  |   |   |   |   |   |   |   |   data <= datain;
40  |   |   |   |   |   |   |   |   elsif (read_sig = '1') then
41  |   |   |   |   |   |   |   |   |   dataout <= data;
42  |   |   |   |   |   |   |   |   |   End if;
43  |   |   |   |   |   |   |   |   End if;
44  |   |   |   |   |   |   |   End process;
45  |   |   |   |   |   |   End Behavioral;
46  |   |
47  |   |
```

Successful Compilation of Memory Component:

memory.vhd		Compilation Report - control_unit	
Table of Contents		Flow Summary	
Flow Summary		<<Filter>>	
Flow Settings		Flow Status	
Flow Non-Default Global Settings		Successful - Mon May 23 00:42:31 2022	
Flow Elapsed Time		Quartus Prime Version	
Flow OS Summary		17.1.0 Build 590 10/25/2017 SJ Lite Edition	
Flow Log		Revision Name	
> Analysis & Elaboration		control_unit	
Flow Messages		Top-level Entity Name	
Flow Suppressed Messages		memory	
		Family	
		MAX 10	
		Device	
		10M08DAF256C7G	
		Timing Models	
		Final	
		Total logic elements	
		N/A until Partition Merge	
		Total registers	
		N/A until Partition Merge	
		Total pins	
		N/A until Partition Merge	
		Total virtual pins	
		N/A until Partition Merge	
		Total memory bits	
		N/A until Partition Merge	
		Embedded Multiplier 9-bit elements	
		N/A until Partition Merge	
		Total PLLs	
		N/A until Partition Merge	
		UFM blocks	
		N/A until Partition Merge	
		ADC blocks	
		N/A until Partition Merge	

Control Unit Component

```
1
2  Library ieee;
3  use ieee.std_logic_1164.all;
4  use ieee.std_logic_arith.all;
5  use ieee.std_logic_unsigned.all;
6  use ieee.std_logic_1164.all;
7
8  entity control_unit is
9  port
10  (
11    clk: in std_logic;
12    IR: in std_logic_vector (31 downto 0);
13    PCout, PCin, MAin, MDout, MDin, MDbus: out std_logic;
14    Cout, Cin, C1out, C2out, Gra, Grb, Grc, CONin, n: out std_logic;
15    IRin, Rout, Rin, Ld: out std_logic;
16    INC4, END_sig, ADD, SUB, OR_sig: out std_logic;
17    Read_sig, Write_sig, Wait_sig, Goto6, C_B, Decr: out std_logic;
18    Ain, Bin, BAout, AND_sig, SHC: out std_logic;
19    Result: out std_logic_vector (4 downto 0)
20  );
21
22  end control_unit;
23
24
25  architecture Behavioral of control_unit is
26    Signal Op: std_logic_vector (4 downto 0);
27    Signal T: integer range 0 to 7 := 0; --steps
28
29  begin
30    Op <= IR(31 downto 27);
31
32    process(clk,Op)
33      Variable x: integer range 0 to 31; --instructions
34
35      Begin
36
37        --Add, Or, Sub, And, Addi , Ld, St, Lar, Br1pl, Br1mi, Stop, Nop, Shc.
38
39    end process;
```

```

40      Case Op is
41      when "00000" => x:= 0; --nop
42      when "00001" => x:= 1; --ld
43      when "00011" => x:= 3; --st
44      when "00110" => x:= 6; --lar
45      when "01100" => x:= 12; --add
46      when "01101" => x:= 13; --addi
47      when "01110" => x:= 14; --sub
48      when "10010" => x:= 18; --brlp
49      when "10011" => x:= 19; --brlmi
50      when "10100" => x:= 20; --and
51      when "10110" => x:= 22; --or
52      when "11101" => x:= 29; --shc
53      when "11111" => x:= 31; --stop
54      when others => null;
55      end case;
56
57      --Output control signals:
58
59
60
61      if (clk'event AND clk = '1') then
62
63          PCout<='0'; PCin<='0'; MAIN<='0'; MDout<='0'; MDin<='0';
64          MDbus<='0'; Cout<='0'; Cin<='0'; Clout<='0'; C2out<='0';
65          Gra<='0'; Grb<='0'; Grc<='0'; CONin<='0'; n<='0';
66          Rout<='0'; IRin<='0'; Rout<='0'; Rin<='0'; Ld<='0';
67          INC4<='0'; END_sig<='0'; ADD<='0'; SUB<='0'; OR_sig<='0';
68          Read_sig<='0'; Write_sig<='0'; Wait_sig<='0'; Goto6<='0'; Ain<='0'; Decr <='0';
69          Bin<='0'; BAout<='0'; OR_sig<='0'; AND_sig<='0'; SHC<='0'; C_B<='0';
70
71
72      if (T = 0 ) then --instruction fetch step 1
73      if (x=0 or x=1 or x=3 or x=6 or x=12 or x=13 or x=14 or x=18 or x=19 or x=20 or x=22 or x=29 or x=31) then
74      PCout<='1'; MAIN<='1'; INC4<='1'; Cin<='1';
75      end if;
76
77
78      elsif (T = 1) then --instruction fetch step 2
79      if (x=0 or x=1 or x=3 or x=6 or x=12 or x=13 or x=14 or x=18 or x=19 or x=20 or x=22 or x=29 or x=31) then
80      Read_sig<='1'; Wait_sig<='1'; Cout<='1'; PCin<='1';
81      end if;
82
83
84      elsif (T = 2) then--instruction fetch step 3
85      if (x=0 or x=1 or x=3 or x=6 or x=12 or x=13 or x=14 or x=18 or x=19 or x=20 or x=22 or x=29 or x=31) then
86      MDout<='1'; IRin<='1';
87      end if;
88
89
90      elsif (T = 3) then
91      If (x=1 or x=3) then Grb<='1'; BAout<='1'; Ain<='1';
92      elsif (x=6) then PCout<='1'; Ain<='1';
93      elsif (x=29) then Clout<='1'; Ld<='1';
94      elsif (x=18 or x=19) then Grc<='1'; Rout<='1'; CONin<='1';
95      elsif (x=12 or x=13 or x=14 or x=20 or x=22) then Grb<='1'; Rout<='1'; Ain<='1';
96      else END_sig<='1';
97      end if;
98
99      elsif (T = 4) then
100      If (x=1 or x=3 or x=13) then C2out<='1'; ADD<='1'; Cin<='1';
101      elsif (x=6) then Clout<='1'; ADD<='1'; Cin<='1';
102      elsif (x=12 or x=20) then Grc<='1'; Rout<='1'; ADD<='1'; Cin<='1';
103      elsif (x=14) then Grc<='1'; Rout<='1'; SUB<='1'; Cin<='1';
104      elsif (x=18 or x=19) then PCout<='1'; Gra<='1'; Rin<='1';
105      elsif (x=22) then Grc<='1'; Rout<='1'; OR_sig<='1'; Cin<='1';
106      elsif (x=29) then n<='1'; Grc<='1'; Rout<='1'; Ld<='1';
107      else END_sig<='1';
108      end if;
109
110      elsif (T = 5) then
111      If (x=1 or x=3) then Cout<='1'; MAIN<='1';
112      elsif (x=6 or x=12 or x=13 or x=14 or x=20 or x=22) then Cout<='1'; Gra<='1'; Rin<='1'; END_sig<='1';
113      elsif (x=29) then Grb<='1'; Rout<='1'; C_B<='1'; Cin<='1';
114      else END_sig<='1';
115      end if;
116
117
118      elsif (T = 6) then
119      If (x=1) then Read_sig<='1'; Wait_sig<='1';
120      elsif (x=3) then Gra<='1'; Rout<='1'; MDbus<='1';
121      elsif (x=29) then n<='1'; Cout<='1'; SHC<='1'; Cin<='1'; Decr<='1'; Goto6<='1';
122      else END_sig<='1';
123      end if;
124
125
126      elsif (t = 7) then
127      If (x=1) then MDout<='1'; Gra<='1'; Rin<='1'; END_sig<='1';
128      elsif (x=3) then Write_sig<='1'; Wait_sig<='1'; END_sig<='1';
129      elsif (x=29) then Cout<='1'; Gra<='1'; Rin<='1'; END_sig<='1';
130      else END_sig<='1';
131      end if;
132
133      T <= T+1;
134      end if;
135      end if;
136      Result<=Op;
137  end process;
138  end behavioral;

```

Successful Compilation of Control Unit Component:

Compilation Report - control_unit		control_unit.vhd	
Table of Contents		Flow Summary	
Flow Summary		<<Filter>>	
Flow Settings		Flow Status	
Flow Non-Default Global Settings		Successful - Mon May 23 02:36:05 2022	
Flow Elapsed Time		Quartus Prime Version	
Flow OS Summary		17.1.0 Build 590 10/25/2017 SJ Lite Edition	
Flow Log		Revision Name	
> Analysis & Elaboration		control_unit	
Flow Messages		Top-level Entity Name	
Flow Suppressed Messages		control_unit	
		Family	
		MAX 10	
		Device	
		10M08DAF256C7G	
		Timing Models	
		Final	
		Total logic elements	
		N/A until Partition Merge	
		Total registers	
		N/A until Partition Merge	
		Total pins	
		N/A until Partition Merge	
		Total virtual pins	
		N/A until Partition Merge	
		Total memory bits	
		N/A until Partition Merge	
		Embedded Multiplier 9-bit elements	
		N/A until Partition Merge	
		Total PLLs	
		N/A until Partition Merge	
		UFM blocks	
		N/A until Partition Merge	
		ADC blocks	
		N/A until Partition Merge	

Data Path Component

```
1
2  Library ieee;
3  use ieee.std_logic_unsigned.all;
4  use ieee.std_logic_1164.all;
5  use ieee.std_logic_arith.all;
6
7  entity Datapath is
8  port(
9      clk_datapath: in std_logic;
10     PCout, PCin, MAin, MDout, MDin, MDbus: in std_logic;
11     Cout, Cin, C1out, C2out, Gra, Grb, Grc, CONin, n: in std_logic;
12     IRin, Rout, Rin, Ld: in std_logic;
13     INC4, END_sig, ADD, SUB, OR_sig: in std_logic;
14     Read_sig, Write_sig, C_B, Decr, Goto6: in std_logic;
15     Ain, Bin, Wait_sig, BAout, AND_sig, SHC: in std_logic;
16     Opcode: out std_logic_vector(4 downto 0));
17 end Datapath;
18
19
20 architecture Behavioral of Datapath is
21
22     COMPONENT ALU is
23     port
24     (
25         clk: in std_logic;
26         Bus_32: in std_logic_vector(31 downto 0);
27         A: in std_logic_vector(31 downto 0);
28         n, ADD, SUB, AND_sig, OR_sig, SHC, C_B, INC4: in std_logic;
29         C: out std_logic_vector(31 downto 0)
30     );
31 end COMPONENT;
32
33
34     COMPONENT register_file is
35     port(
36         Rin: in std_logic;
37         Gra: in std_logic;
38         Grb: in std_logic;
39         Grc: in std_logic;
40         Rout: in std_logic;
41         BAout: in std_logic;
42         IR: in std_logic_vector(31 downto 0);
43         Bus_32_in: in std_logic_vector(31 downto 0);
44         Bus_32_out: out std_logic_vector(31 downto 0)
45     );
46 end COMPONENT;
47
```

```

48 |
49 | COMPONENT memory is
50 | port(
51 |   clk: in std_logic;
52 |   MAin: in std_logic;
53 |   MDin, MDout, write_sig, read_sig: in std_logic;
54 |   datain: in std_logic_vector(31 downto 0); --input of MA
55 |   datain1: in std_logic_vector(31 downto 0);
56 |   dataout: out std_logic_vector(31 downto 0); --output of MA
57 |   dataout1: out std_logic_vector(31 downto 0)
58 | );
59 | end COMPONENT;
60 |
61 | COMPONENT control_unit is
62 | port
63 | (
64 |   clk: in std_logic;
65 |   IR: in std_logic_vector(31 downto 0);
66 |   PCout, PCin, MAin, MDout, MDin, MDbus: out std_logic;
67 |   Cout, Cin, Clout, C2out, Gra, Grb, Grc, CONin, n: out std_logic;
68 |   IRin, Rout, Rin, Ld: out std_logic;
69 |   INC4, END_sig, ADD, SUB, OR_sig: out std_logic;
70 |   Read_sig, Write_sig, Wait_sig, Goto6, C_B, Decr: out std_logic;
71 |   Ain, Bin, BAout, AND_sig, SHC: out std_logic;
72 |   Result: out std_logic_vector(4 downto 0)
73 | );
74 | end COMPONENT;
75 |
76 | Signal A_sig: std_logic_vector(31 downto 0) := x"00001111";
77 | Signal C_sig: std_logic_vector(31 downto 0) := x"00000000";
78 | Signal MainBus: std_logic_vector(31 downto 0) := x"00000000"; --datain
79 | Signal MainBus2: std_logic_vector(31 downto 0) := x"00000000"; --datain1
80 | Signal BusTemp: std_logic_vector(31 downto 0) := x"00000000"; --dataout
81 | Signal BusTemp1: std_logic_vector(31 downto 0) := x"00000000"; --dataout1
82 | Signal IR_sig: std_logic_vector(31 downto 0) := x"00000000";
83 | Signal PCout_sig, PCin_sig, MAin_sig, MDout_sig, MDin_sig, MDbus_sig,
84 |   Cout_sig, Cin_sig, Clout_sig, C2out_sig, Gra_sig, Grb_sig, Grc_sig,
85 |   CONin_sig, n_sig, IRin_sig, Rout_sig, Rin_sig, Ld_sig, INC4_sig, END_i, ADD_sig, SUB_sig, OR_i, Read_i, Write_i,
86 |   Wait_i, Goto6_sig, C_B_sig, Decr_sig, Ain_sig, Bin_sig, BAout_sig, AND_i, SHC_sig: std_logic;
87 |
88 |
89 | Begin
90 |
91 |
92 | u0: ALU port map (clk_datapath, MainBus, A_sig, n, ADD, SUB, AND_sig,
93 |   OR_sig, SHC, C_B, INC4, C_sig);
94 |
95 |
96 | u1: register_file port map (Rin, Gra, Grb, Grc, Rout, BAout, IR_sig, MainBus, BusTemp1);
97 |
98 |
99 | u2: memory port map (clk_datapath, MAin, MDin, MDout, Write_sig, Read_sig,
100 |   MainBus, MainBus2, BusTemp, BusTemp1);
101 |
102 |
103 | u3: control_unit port map (clk_datapath, IR_sig,
104 |   PCout_sig, PCin_sig, MAin_sig, MDout_sig, MDin_sig, MDbus_sig,
105 |   Cout_sig, Cin_sig, Clout_sig, C2out_sig, Gra_sig, Grb_sig, Grc_sig,
106 |   CONin_sig, n_sig, IRin_sig, Rout_sig, Rin_sig, Ld_sig, INC4_sig,
107 |   END_i, ADD_sig, SUB_sig, OR_i, Read_i, Write_i,
108 |   Wait_i, Goto6_sig, C_B_sig, Decr_sig, Ain_sig, Bin_sig, BAout_sig, AND_i, SHC_sig, Opcode);
109 |
110 | end Behavioral;
111 |

```

Successful Compilation of Data Path Component:

Compilation Report - control_unit

Datapath.vhd

Table of Contents

Flow Summary

Flow Settings

Flow Non-Default Global Settings

Flow Elapsed Time

Flow OS Summary

Flow Log

Analysis & Elaboration

Flow Messages

Flow Suppressed Messages

<<Filter>>


Flow Status	Successful - Mon May 23 02:39:42 2022
Quartus Prime Version	17.1.0 Build 590 10/25/2017 SJ Lite Edition
Revision Name	control_unit
Top-level Entity Name	Datapath
Family	MAX 10
Device	10M08DAF256C7G
Timing Models	Final
Total logic elements	N/A until Partition Merge
Total registers	N/A until Partition Merge
Total pins	N/A until Partition Merge
Total virtual pins	N/A until Partition Merge
Total memory bits	N/A until Partition Merge
Embedded Multiplier 9-bit elements	N/A until Partition Merge
Total PLLs	N/A until Partition Merge
UFM blocks	N/A until Partition Merge
ADC blocks	N/A until Partition Merge

Results


This section will focus on the RTN and simulation results obtained from each and every component.

Components RTL


ALU Unit Component

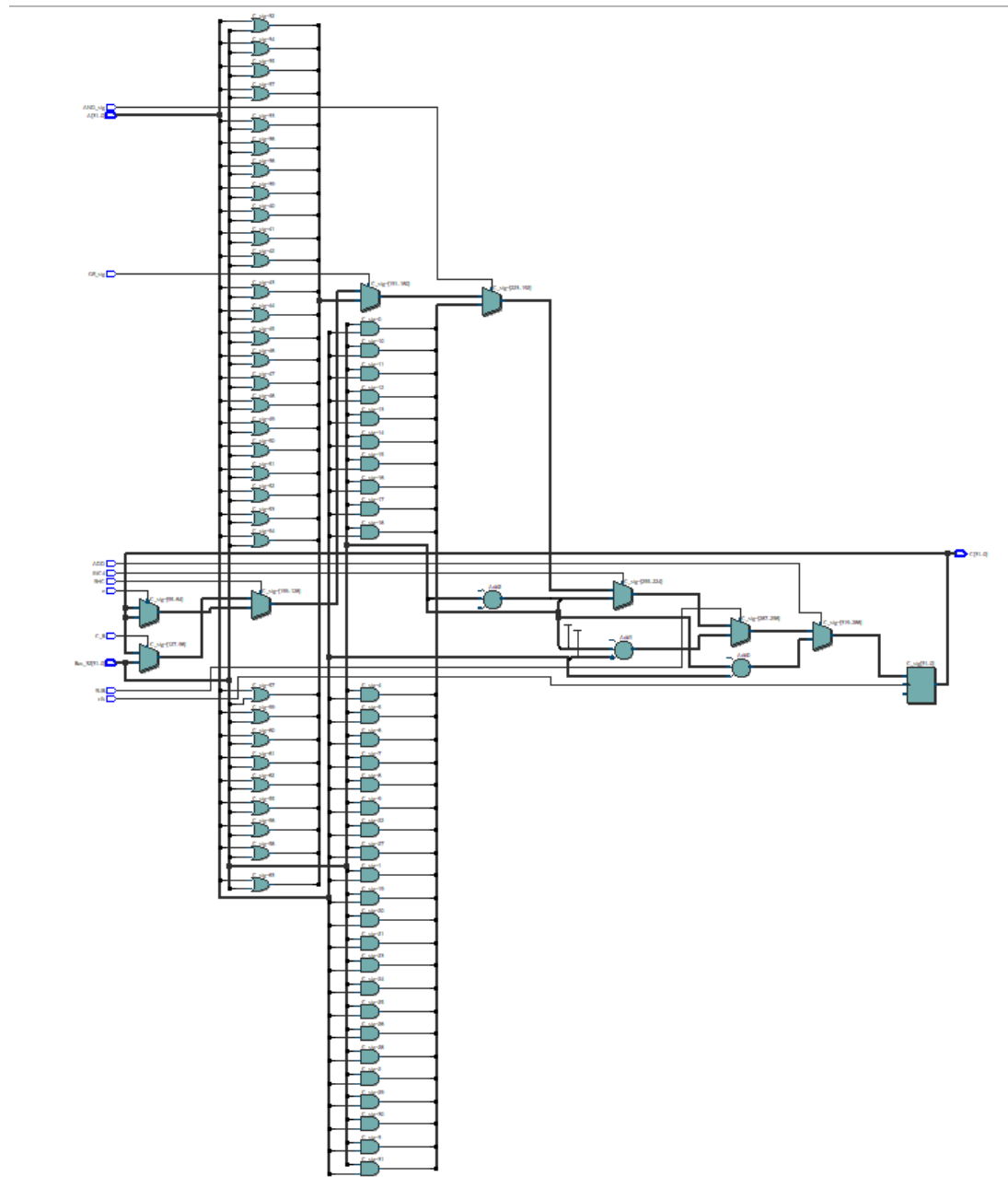


Closer Look at ALU Component RTL Viewer:

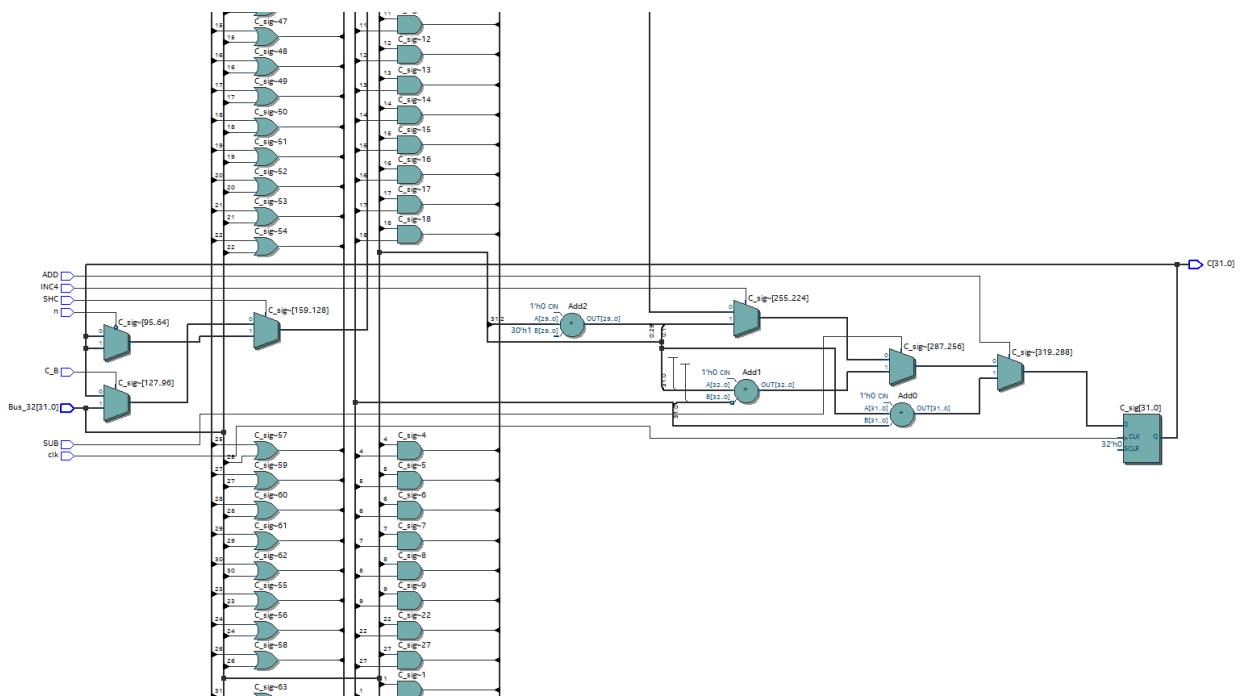


Memory Unit Component

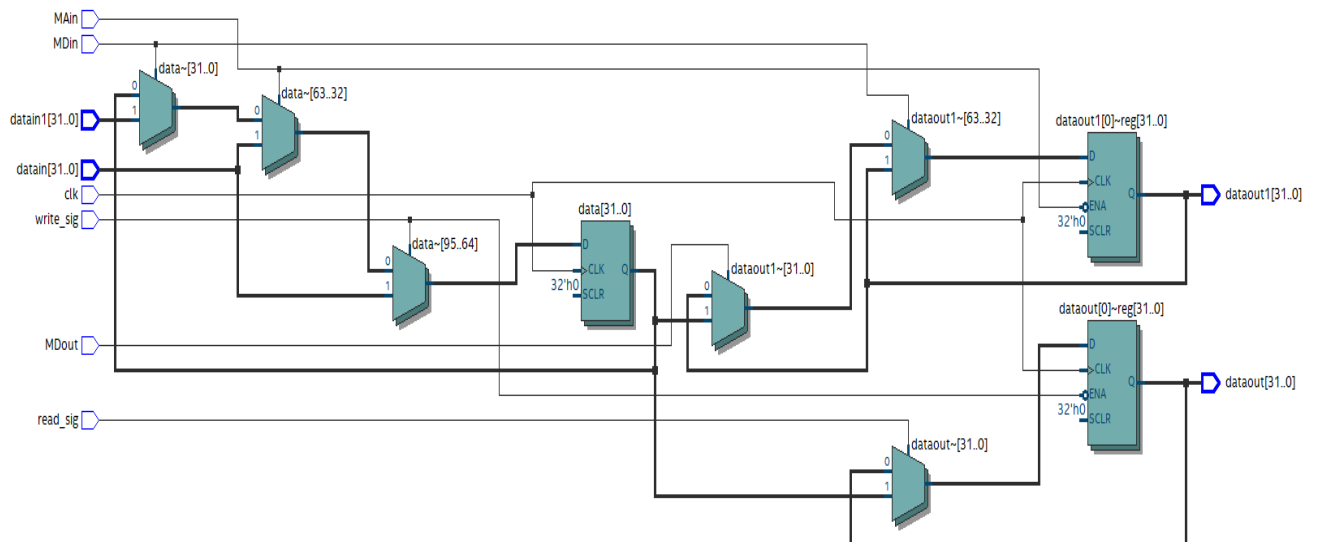


Register File Component

 

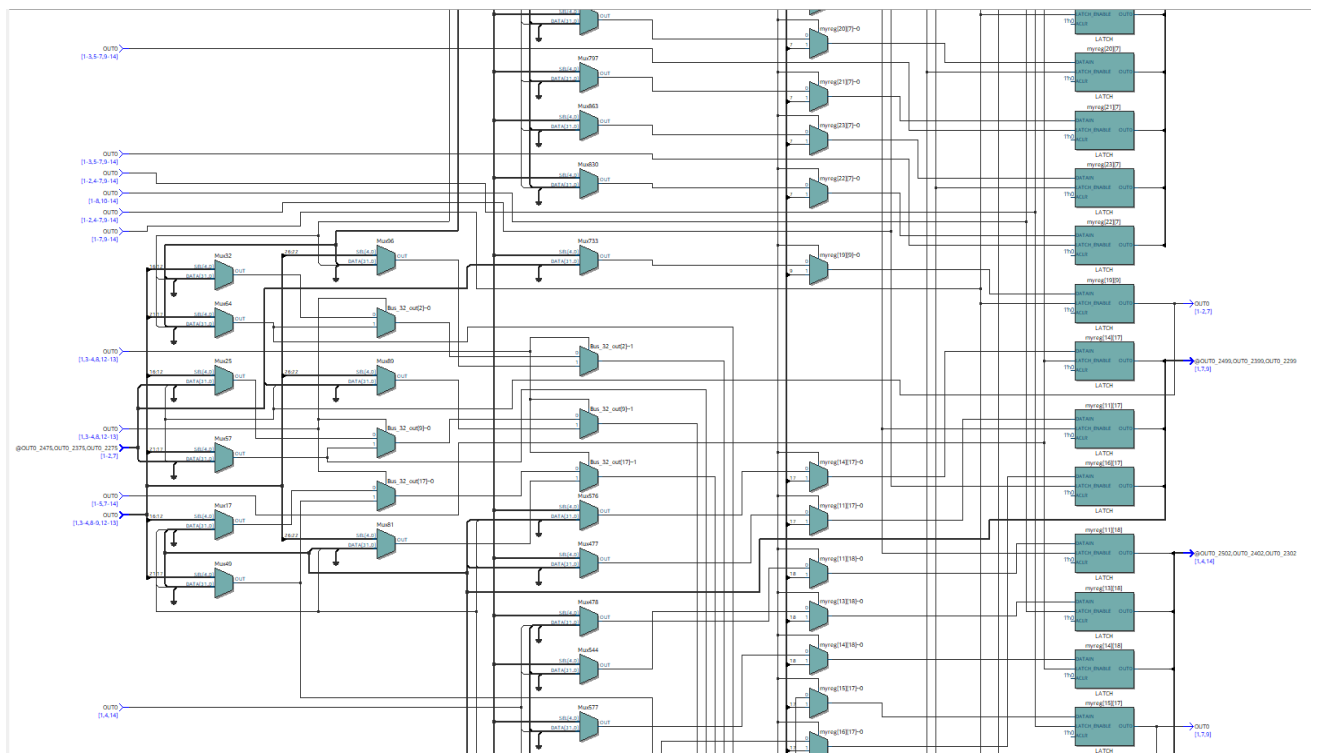
Closer Look at Register File Component RTL Viewer:




Control Unit Component

 

 Closer Look at Control Unit Component RTL Viewer:





Data Path Component

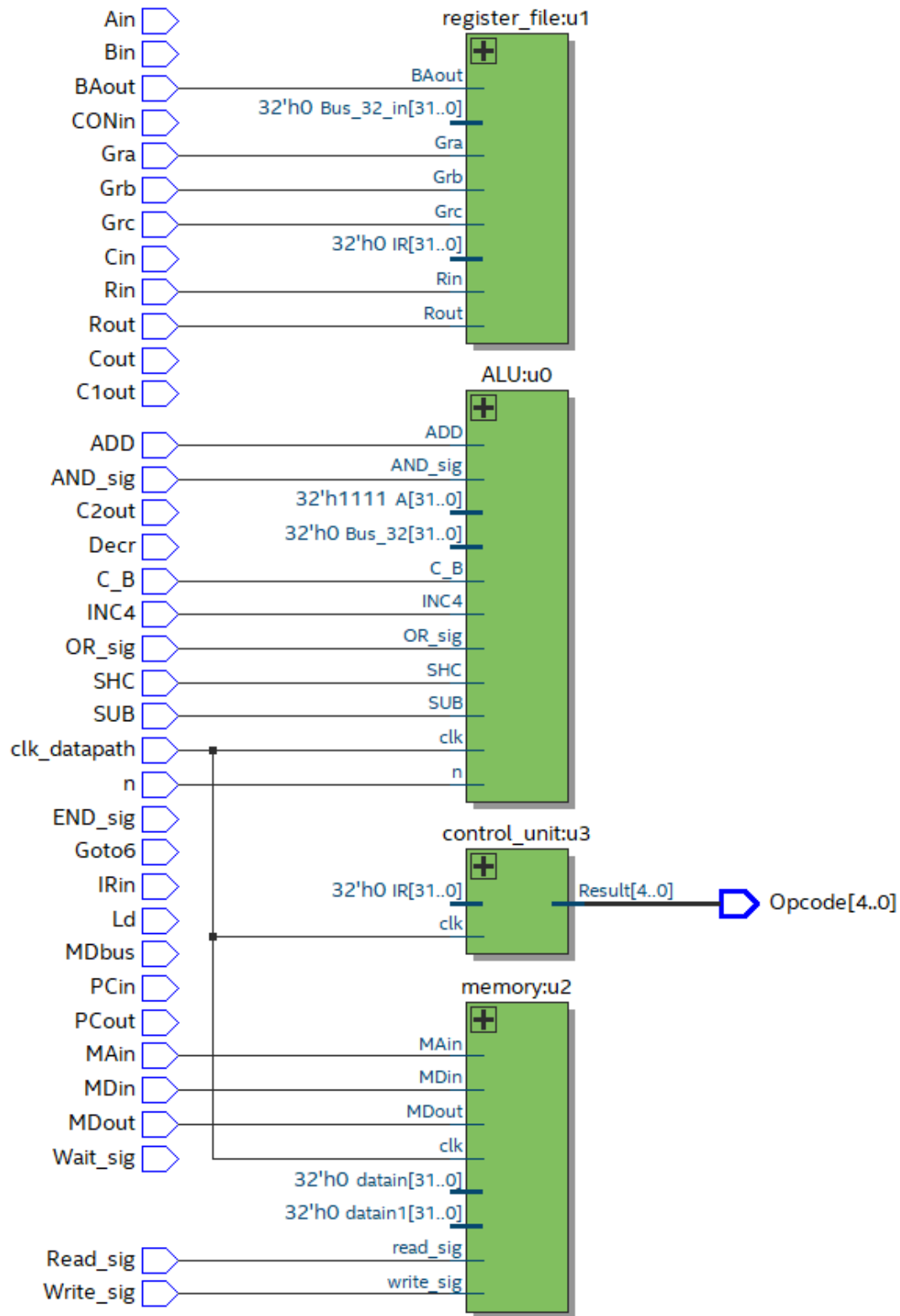

Components Simulation

ALU Unit Component

  

The following inputs were initialized:

Bus_32: 00010101 01011111 11111100 00011010 (binary) = 155FFC1A (hexadecimal)

A: 00010101 01011111 11111100 00001011 (binary) = 155FFC0B (hexadecimal)

At 1st clock pulse: (Addition operation)

When ADD=1, we get output C= 2ABFF825 (hexadecimal)

At 2nd clock pulse: (Subtraction operation)


When SUB=1, we get output C= F (hexadecimal)

At 3rd clock pulse: (AND operation)

When AND=1, we get output C= 155FFC0A (hexadecimal)

In case of Shift Circular operation:

 When SHC=1, n=1 (at each clock pulse the LSB from the existing output shifts in the below manner)



Before 4th clock pulse: 0001010101011111111110000001010 = 155FFC0A (hexadecimal)

After 4th clock pulse: 00101010101111111111100000010100 = 2ABFF814 (hexadecimal)

After 5th clock pulse: 010101010111111111111000000101000 = 557FF028 (hexadecimal)

After 6th clock pulse: 1010101011111111111110000001010000 = AAFFE050 (hexadecimal)

At 7th clock pulse: (INC4 operation)


When INC4=1, we get output C= 00010101010111111111110000011010 = 155FFC1E (hexadecimal)

At 8th clock pulse: (C_B operation)

When C_B =1, we get output C= 155FFC1A (hexadecimal)

Register File Component

 The beginning phase when we can see the signal initialised for the 24 General Purpose Registers




The following inputs were initialized:


Bus_32_in: 00010101 01011111 11111100 00011010 (binary) = 155FFC1A (hexadecimal)

IR: 00010101 01011111 11111100 00001011 (binary) = 155FFC0B (hexadecimal)


Condition 1: When Rin=1, Gra=1, we save the value of the (Bus_32_in) input to one of the register signals

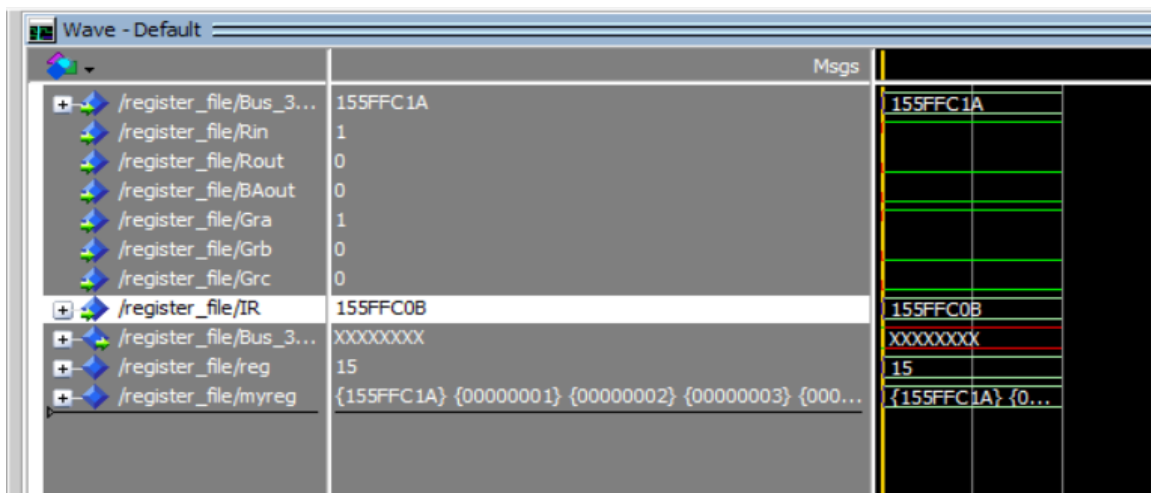

Condition 2: When Rout=1, Gra=1, we get the value saved in the register as (Bus_32_out) output

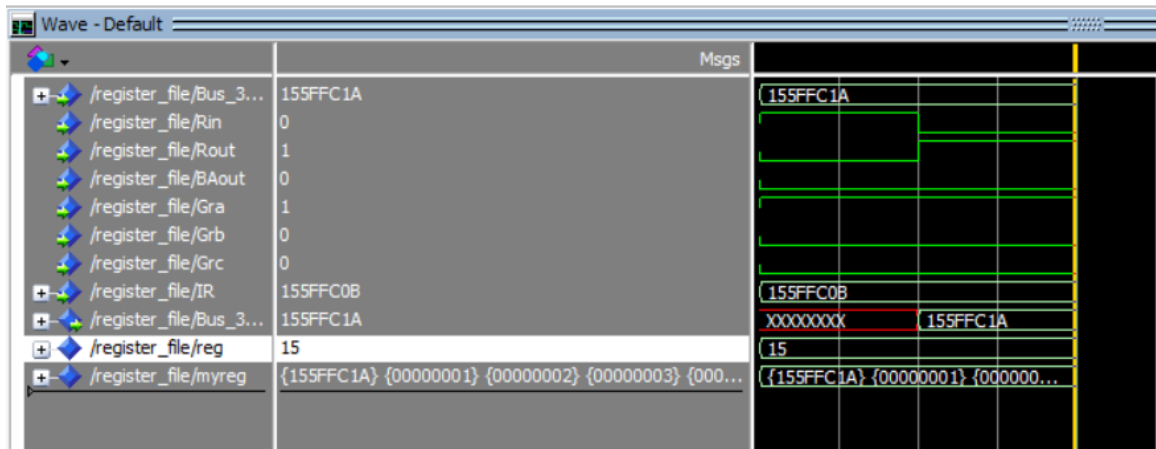

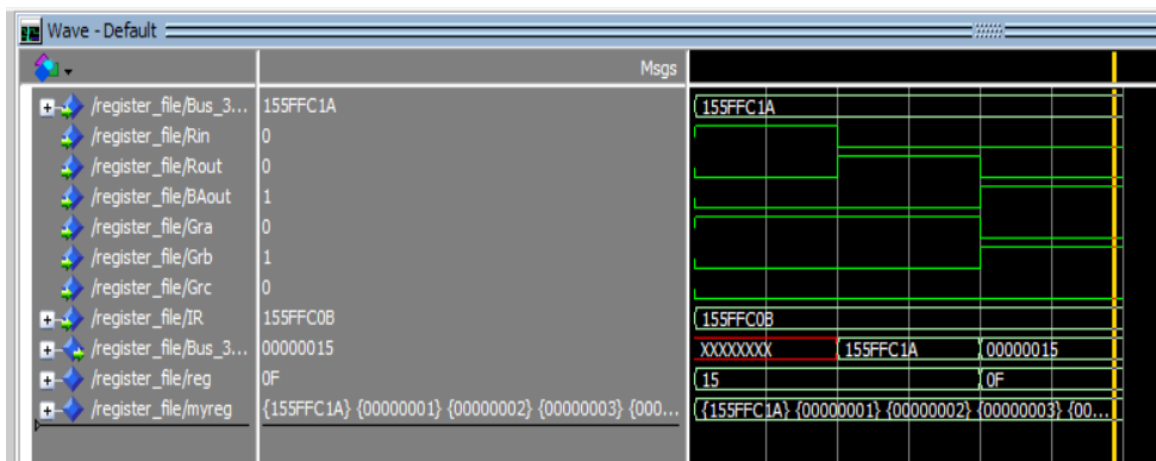Condition 3: When BAout=1, Grb=1 we get the value from IR(21 downto 17)= 01111 (binary)= 15 (decimal) as output for (Bus_32_out)



Memory Unit Component

The following inputs were initialized:

Datain: 155FFC1A (hexadecimal)

Datain1: 155FFC0B (hexadecimal)



At rising edge of clock when Main=1, we get data signal = 155FFC1A (hexadecimal)

When MDin=1, we get data signal = 155FFC0B (hexadecimal)

When MDout=1, we get Dataout1 = 155FFC0B (previously saved as data signal)

When Write=1, we get data signal = Datain = 155FFC1A (hexadecimal)

 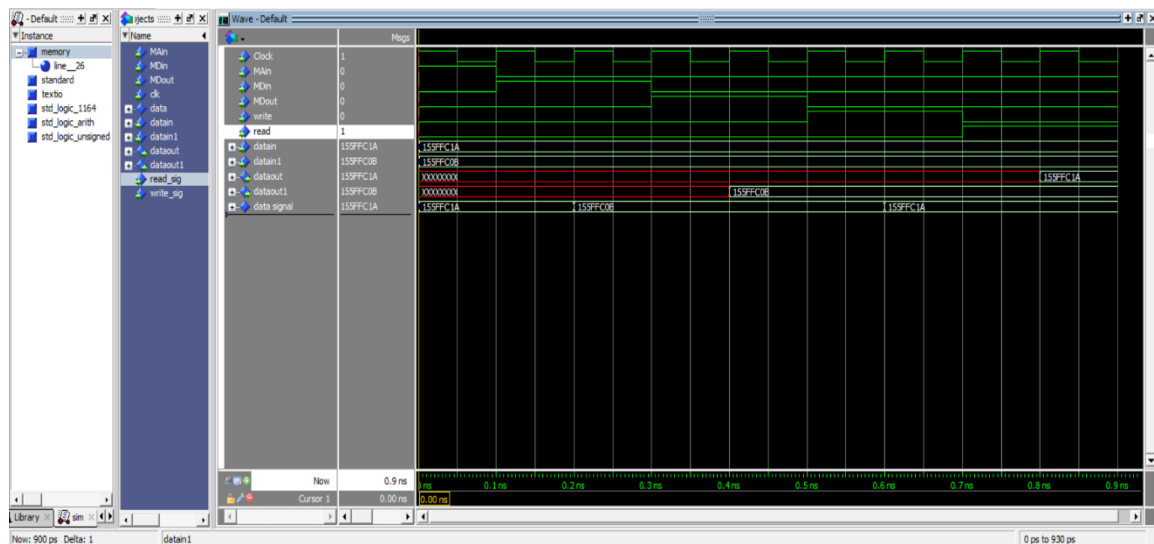When Read=1, we get Dataout = 155FFC1A (hexadecimal) (previously inputted using write signal)




Control Unit Component


The following inputs were initialized:

IR: 00010101 01011111 11111100 00001011 (binary) = 155FFC0B (hexadecimal)

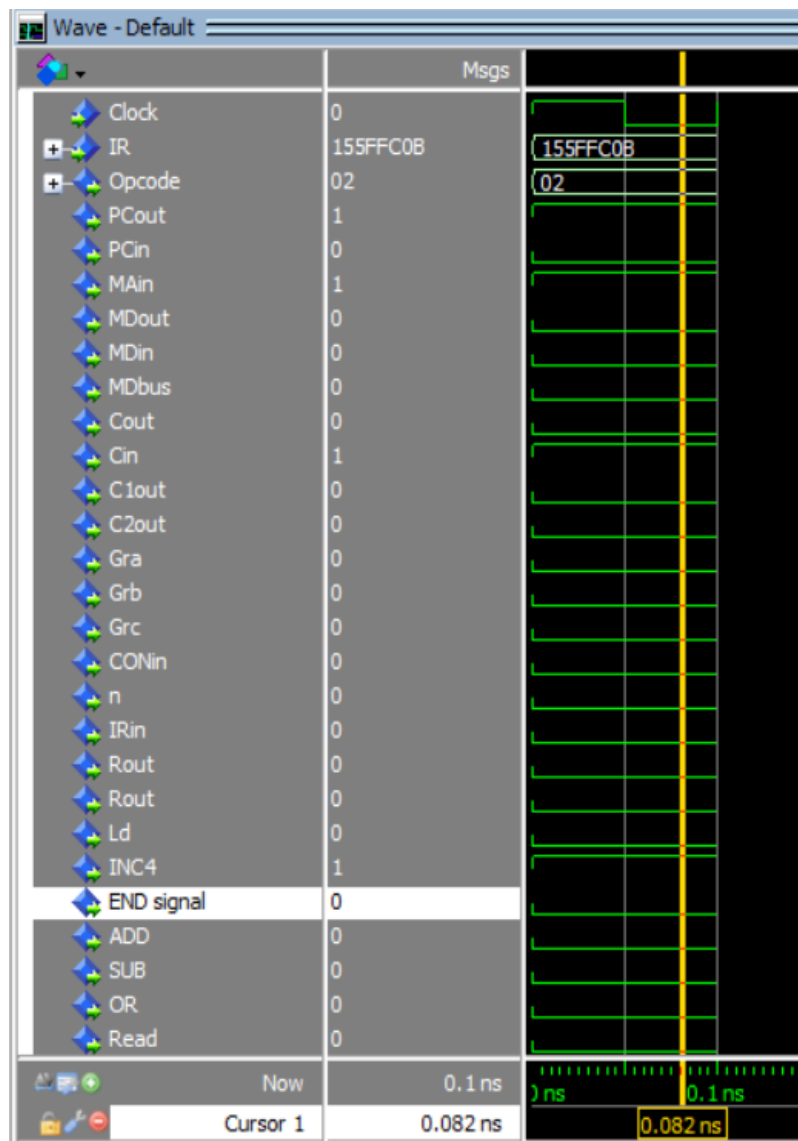The following outputs were obtain PCout=1, Main=1, INC4=1, Cin=1, Opcode=2 (decimal) and initially step T=0 ([instruction fetch step 1](#))




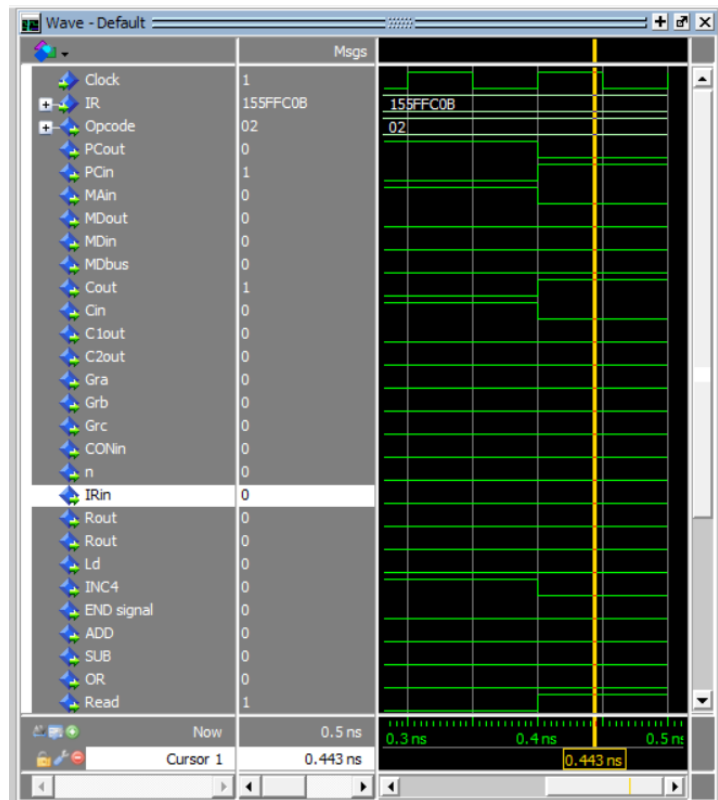To verify the simulation, we manually initialized step T=1 ([instruction fetch step 2](#)) to match with control unit outputs Read=1, Wait=1, Cout=1, PCin=1, Opcode=2 (decimal)




We initialised an input where IR: 01100101 01011111 11111100 00001011 (binary) = 655FFC0B (hexadecimal)

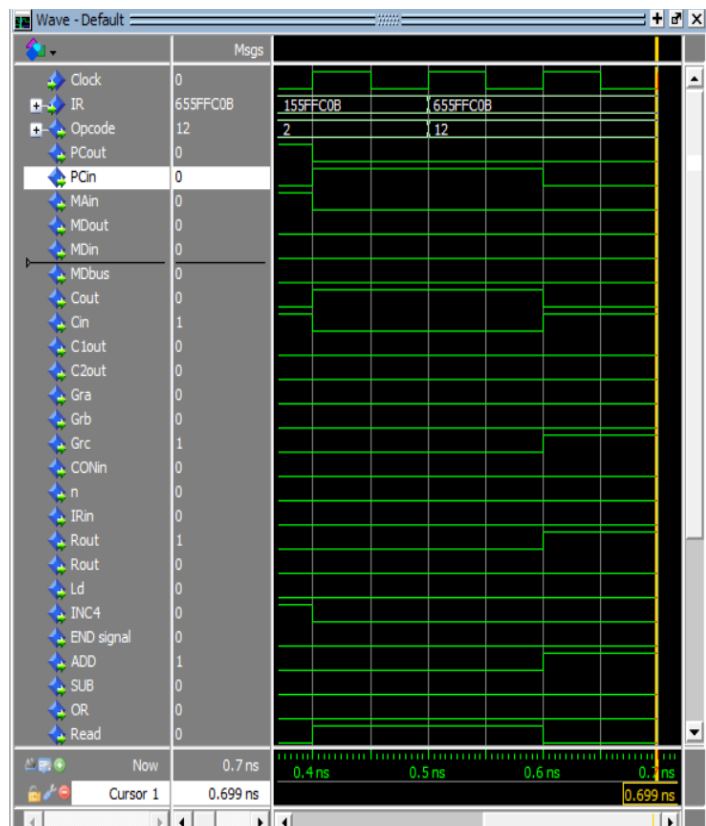We get outputs Grc=1, Rout=1, ADD=1, Cin=1, Opcode=12 (decimal) which is [ADD operation](#) and set the step T=4 to verify the simulation.




We initialised an input where IR: FD5FFC0B (hexadecimal)

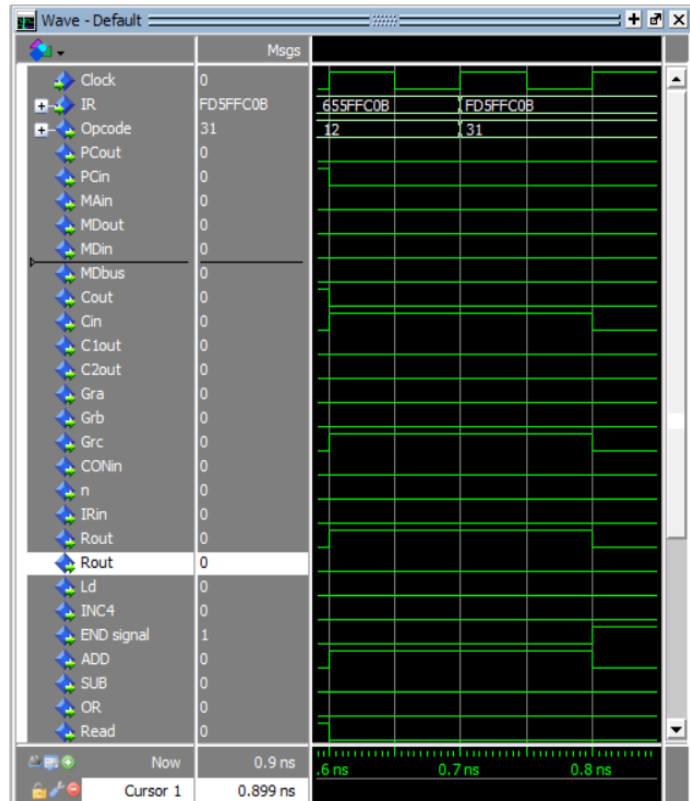We get all outputs zero other than End_signal=1, Opcode=31 (decimal) which is [STOP operation](#) and set the step T=4 to verify the simulation.




We initialised an input where IR: 355FFC0B (hexadecimal)

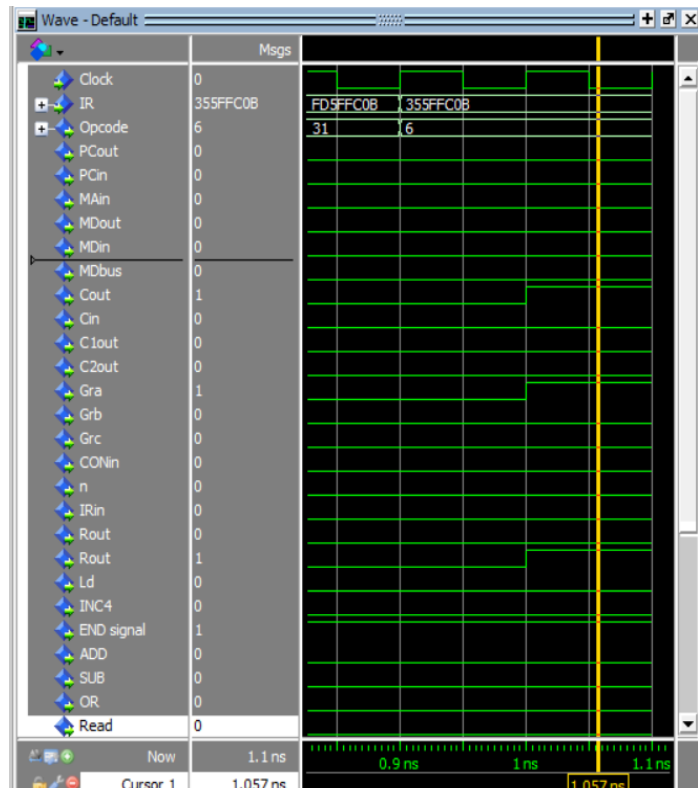We get as outputs Cout=1, Gra=1, Rin=1, END_signal=1, Opcode=6 (decimal) which is [LAR operation](#) and set the step T=5 to verify the simulation.



We initialised an input where IR: 955FFC0B (hexadecimal)

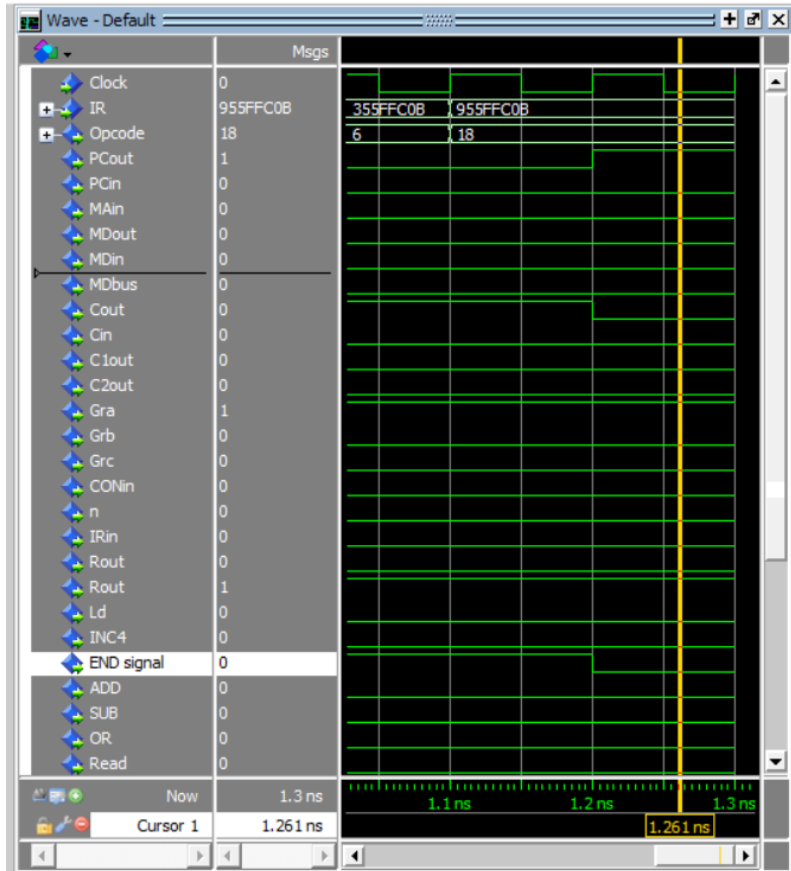We get as outputs PCout=1, Gra=1, Rin=1, Opcode=18 (decimal) which is [brlpl operation](#) and set the step T=4 to verify the simulation.



Conclusion

The objective of this project have been achieved by implementing implement 1-bus processor with a hardwired control unit that have specific characteristic using VHDL Code. Also, the components' functionality was tested by running the RTL Viewer and simulate each component. Furthermore, we have tried to connect all components as a one system. By achieving these goals, the team members have learnt:

- The importance of RTN Concrete (Control Signals) within the CPU.
- Learnt how to program all the components and debug errors.
- Understand how all the components are connected to reach other and how we program the top level.
- Main program syntax was learnt for example, during the use of “while” condition the ‘process’ is not required.